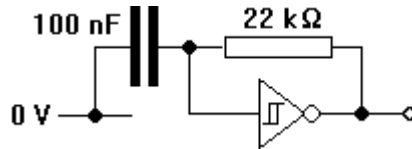



Designing a falling-edge-to-pulse converter

You are going to design a circuit which produces a single $50\ \mu\text{s}$ pulse each time a falling-edge enters it.

1. Assemble the relaxation oscillator shown below. Run the 40106 Schmitt trigger inverter off supply rails at +5 V and 0 V.



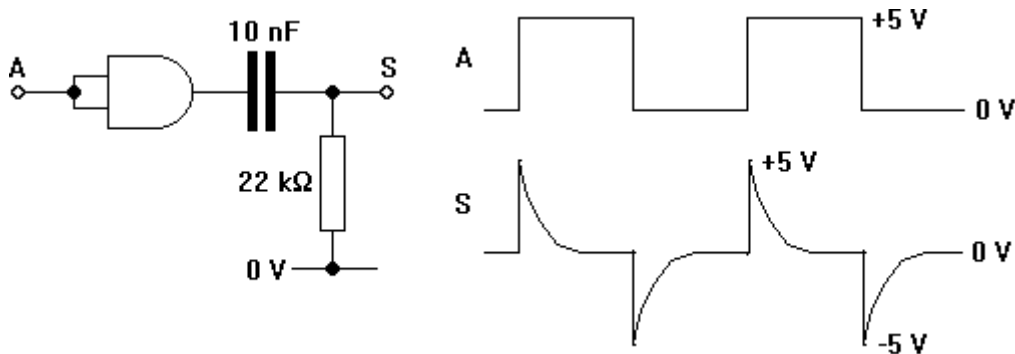2. Use a CRO to verify that the oscillator feeds out a square wave with a frequency of about 1 kHz.
3. Assemble the circuit shown below. Connect A to the output of the oscillator and S to the second input of the CRO. Verify that the waveforms at A and S are as shown below.



4. Connect both inputs of an AND gate to S and look at its output with the CRO. Verify that it produces a single $0.15\ \text{ms}$ pulse at every rising edge at A.
5. Adapt the circuit so that it produces a $50\ \mu\text{s}$ pulse on each falling edge at A.